8:1 MUX

.vhd File Code


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux is
 Port (sel: in STD_LOGIC_VECTOR (2
      downto 0); inp: in
      STD_LOGIC_VECTOR (7 downto 0);
      DIS: out STD LOGIC VECTOR (1 downto 0);
      led p: out STD LOGIC VECTOR (3 downto 0);
      led n: out STD LOGIC VECTOR (3 downto 0);
      SEG: out STD LOGIC VECTOR (6
downto 0)); end mux;
architecture Behavioral of
mux is begin
     led n (3 downto 1) <= "111";</pre>
     led p(3 downto 0) <="0001";</pre>
     DIS <= "10";
     with sel select
           led n(0) \leftarrow (not inp(0))
           when "000", (not inp (1))
           when "001",
           (not inp (2)) when "010",
           (not inp (3)) when "011",
           (not inp(4)) when "100",
           (not inp (5)) when "101",
           (not inp (6)) when "110",
           (not inp (7)) when
           "111", 'Z' when
           others;
--Display--
     with sel select
```


```
SEG <=
"1000000" when "000",
"1111001" when "001",
"0100100" when "010",
"0110000" when "011",
"0011001" when "100",
"0000010" when "110",
"1111000" when "111",
"0000000" when others;
end Behavioral;
```

.ucf File Code

```
Net "DIS<0>" loc = "p141";
Net "DIS<1>" loc = "p144";
Net "SEG<0>" loc= "p148";
Net "SEG<1>" loc = "p147";
Net "SEG<2>" loc = "p146";
Net "SEG<3>" loc="p143";
Net "SEG<4>" loc = "p140";
Net "SEG<5>" loc = "p138";
Net "SEG<6>" loc = "p139";
Net "led_n<0>" loc = "p132";
Net "led n<1>" loc = "p131";
Net "led_n<2>" loc = "p130";
Net "led_n<3>" loc = "p128";
Net "led_p<0>" loc = "p126";
Net "led_p<1>" loc = "p133";
Net "led p<2>" loc = "p135";
Net "led_p<3>" loc = "p137";
Net "inp<0>" loc = "p101";
Net "inp<1>" loc = "p100";
Net "inp<2>" loc = "p97";
Net "inp<3>" loc = "p96";
Net "inp<4>" loc = "p95";
Net "inp<5>" loc = "p94";
Net "inp<6>" loc = "p93";
Net "inp<7>" loc = "p90";
Net "sel<0>" loc = "p87";
Net "sel<1>" loc = "p86";
Net "sel<2>" loc = "p85";
```

Simulation and RTL Schematic

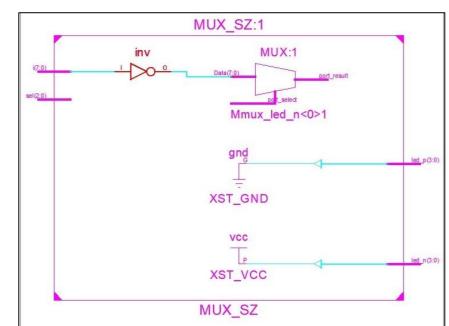

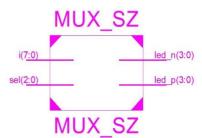

Name	Value	 1,999,992 ps	1,999,993 ps	1,999,994 ps	1,999,995 ps	1,999,996 ps	1,999,997 ps	1,999,998 ps	1,999,999 ps
▶ 🕌 i[7:0]	11000011				11000011				
▶ 🛂 sel[2:0]	001				001				
▶ 🛂 led_p[3:0]	0001				0001				
▶ 🛂 led_n[3:0]	1110				1110				



inp = 00001111 sel = 110



inp = 00001111 sel = 011