

SR Flip-Flop




.vhd file code -

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Combinational is
    Port ( led_p : out STD_LOGIC_VECTOR (3
        downto 0); led_n : out STD_LOGIC_VECTOR
        (3 downto 0); inp : in STD_LOGIC_VECTOR
        (1 downto 0);
        Q : in STD_LOGIC);
end Combinational;
architecture Behavioral of
    Combinational is
begin
    led_p(3 downto 0) <= "0001";
    led_n(3 downto 1) <=
        "111"; with inp select
        led_n(0) <= (not Q) when
        "00", ('1') when "01",
        ('0') when "10",
        'Z' when
others; end
Behavioral;
```


.ucf File Code –

```
Net "led_n<0>" loc = "p132";
Net "led_n<1>" loc = "p131";
Net "led_n<2>" loc = "p130";
Net "led_n<3>" loc = "p128";
Net "led_p<0>" loc = "p126";
Net "led_p<1>" loc = "p133";
Net "led_p<2>" loc = "p135";
Net "led_p<3>" loc = "p137";
Net "inp<0>" loc = "p101";
Net "inp<1>" loc = "p100";
Net "Q" loc = "p97";
```


Simulation and RTL Schematic

 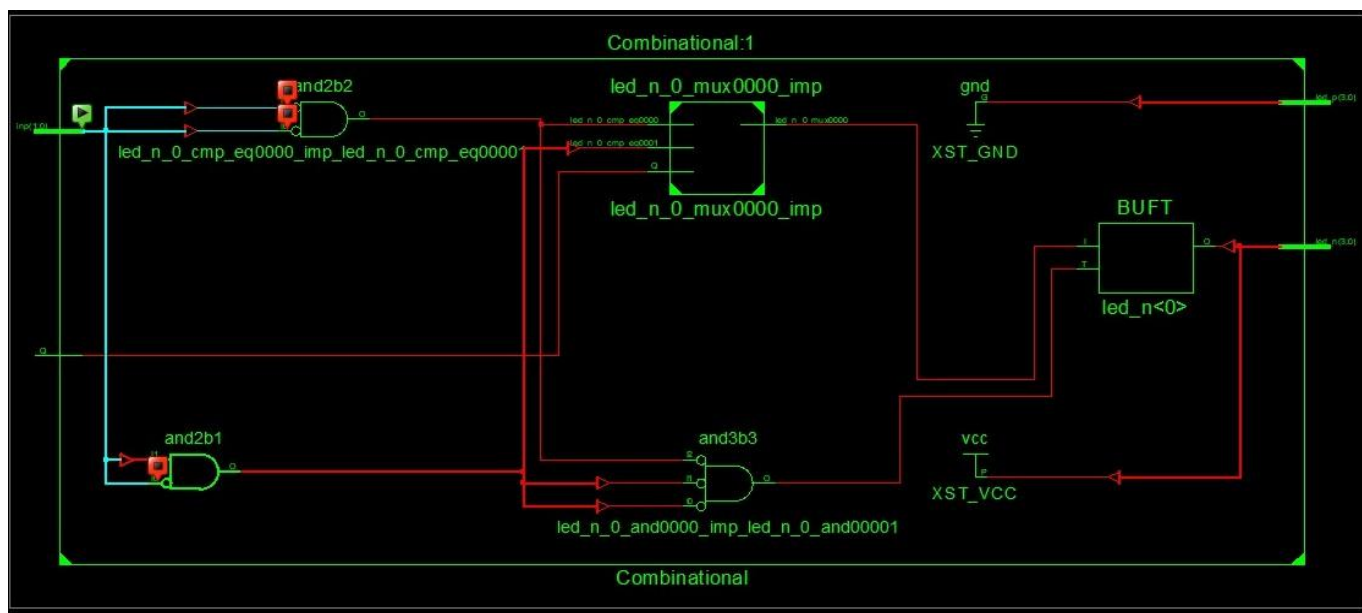 


Kit Output:

 


Hold – inp=11; Q=0

 

Invalid – Q=0; inp=00

 

Set – inp=10; Q=1

 

Reset – inp=01; Q=1

T Flip-Flop




.vhd file Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity T_ff is
    Port (t : in STD_LOGIC; q : in STD_LOGIC;
          led_p : out STD_LOGIC_VECTOR (3 downto 0);
          led_n : out STD_LOGIC_VECTOR (3 downto 0));
end T_ff;
architecture Behavioral of T_ff is
begin
    led_p(3 downto 0) <= "0001";
    led_n(3 downto 1) <= "111"; led_n(0) <= not(t xor q);
end Behavioral;
```


.ucf file code

```
Net "led_n<0>" loc = "p132";
Net "led_n<1>" loc = "p131";
Net "led_n<2>" loc = "p130";
Net "led_n<3>" loc = "p128";
Net "led_p<0>" loc = "p126";
Net "led_p<1>" loc = "p133";
Net "led_p<2>" loc = "p135";
Net "led_p<3>" loc = "p137";
Net "t" loc = "p101";
Net "t" loc = "p100";
```


Simulation and RTL Schematic

 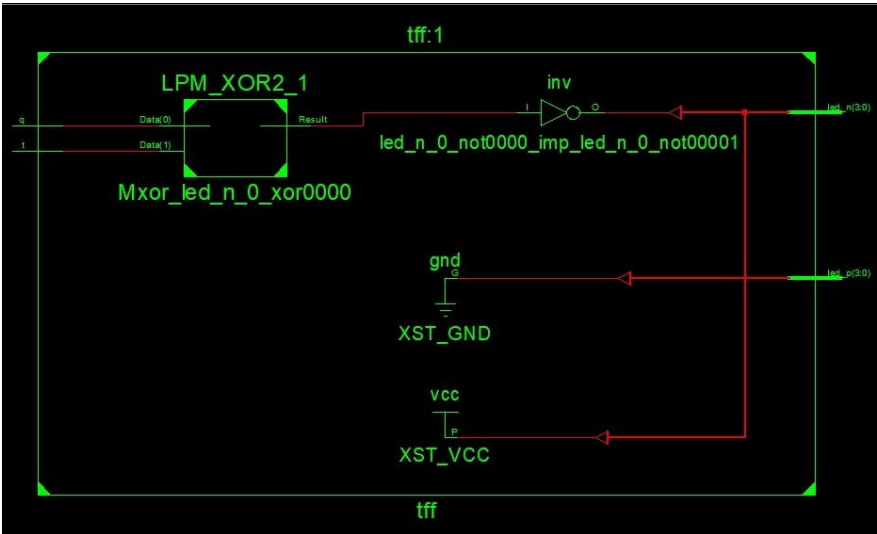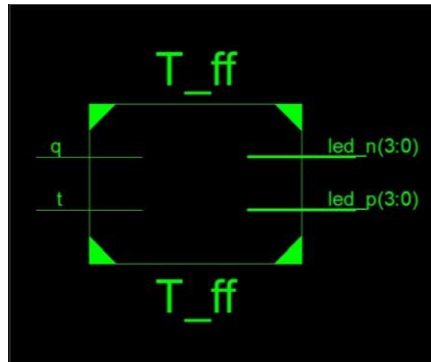

Kit Output:

 

HOLD - Q=1; T=0

 

TOGGLE - Q=0; T=1

JK Flip-Flop




.vhd file Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity JK_FF is
    Port (inp : in STD_LOGIC_VECTOR(1 downto 0);
          Q : in STD_LOGIC;
          led_n : out STD_LOGIC_VECTOR(3 downto 0);
          led_p : out STD_LOGIC_VECTOR(3 downto 0));
end JK_FF;
architecture Behavioral of JK_FF
is
begin
    led_n (3 downto 1) <= "111";
    led_p (3 downto 0) <= "0001";
    with inp select
        led_n(0) <= (not Q)
        when "00", ('0') when
            "01",
            ('1') when "10",
            (Q) when
                "11", 'Z'
        when others;
end Behavioral;
```

.ucf file Code

```
Net "led_n<0>" loc = "p132";
Net "led_n<1>" loc = "p131";
Net "led_n<2>" loc = "p130";
Net "led_n<3>" loc = "p128";
Net "led_p<0>" loc = "p126";
Net "led_p<1>" loc = "p133";
Net "led_p<2>" loc = "p135";
Net "led_p<3>" loc = "p137";
Net "inp<0>" loc = "p101";
Net "inp<1>" loc = "p100";
Net "Q" loc = "p97";
```


Simulation and RTL Schematic

 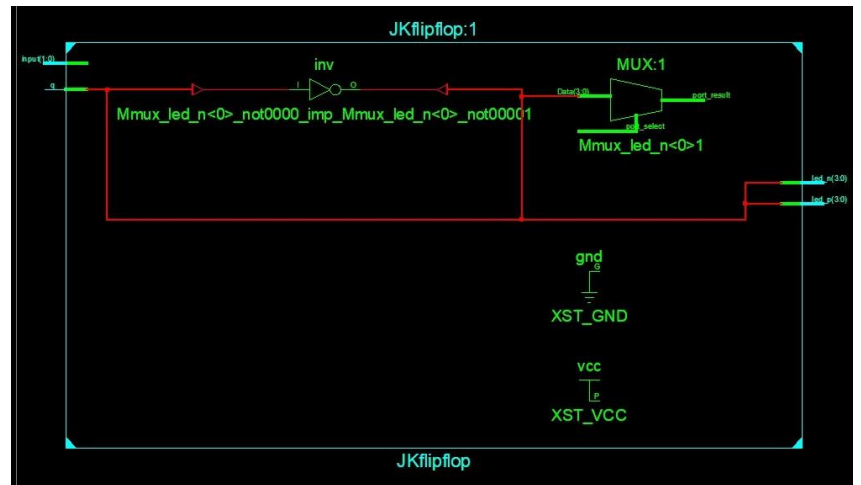 

Kit Output:




HOLD – inp=00; Q=1




TOGGLE – inp=11; Q=0



TOGGLE – inp=11; Q=1

 

RESET – inp = 01; Q = 1

 

SET – inp = 10; Q = 0


D_FF.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity D_FF is
Port (led_n : out STD_LOGIC_VECTOR (3 downto 0);
      led_p : out STD_LOGIC_VECTOR (3 downto 0)
      D : in STD_LOGIC);
end D_FF;
architecture Behavioral of D_FF is
begin
    led_n (3 downto 1) <= "111";
    led_p (3 downto 0) <= "0001";
    process(D)
    begin
        led_n(0) <=
        not(D); end
    process;
end behavioral;
```

D_FF.ucf

```
Net "led_n<0>" loc = "p132";
Net "led_n<1>" loc = "p131";
Net "led_n<2>" loc = "p130";
Net "led_n<3>" loc = "p128";
Net "led_p<0>" loc = "p126";
Net "led_p<1>" loc = "p133";
Net "led_p<2>" loc = "p135";
Net "led_p<3>" loc = "p137";
Net "D" loc = "p87";
```

Simulation and RTL Schematic

 

Kit Output:



D = 1; Q = 1



D = 0; Q = 0