
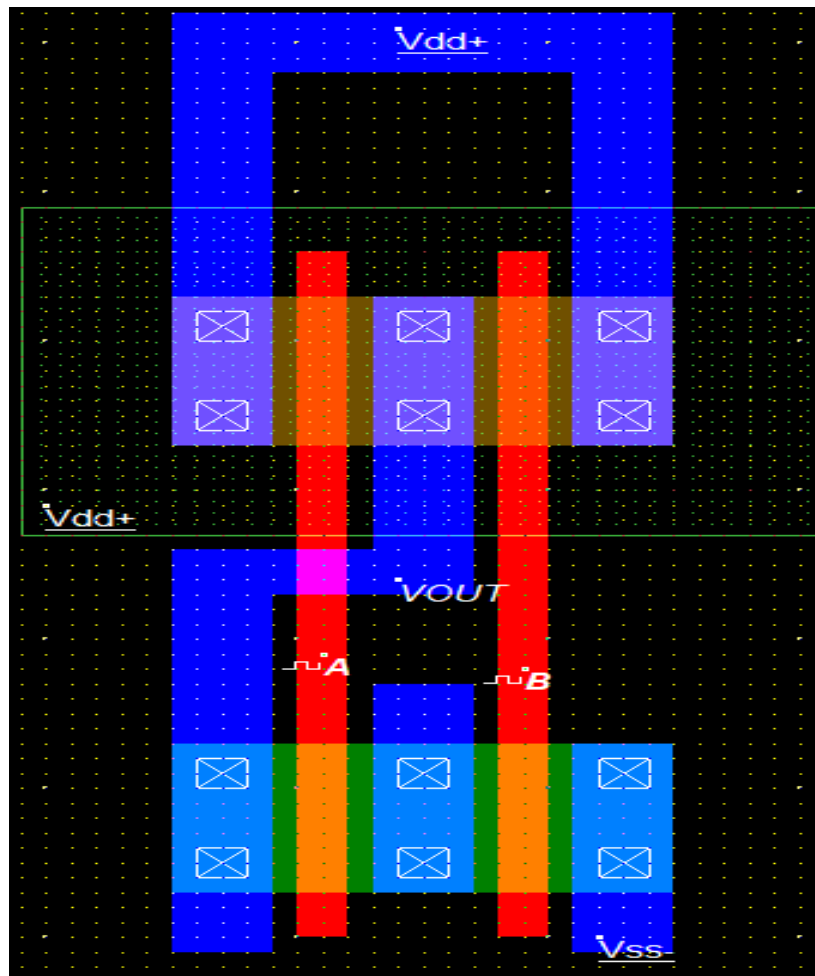


NAND Gate using PMOS and NMOS –

Design –

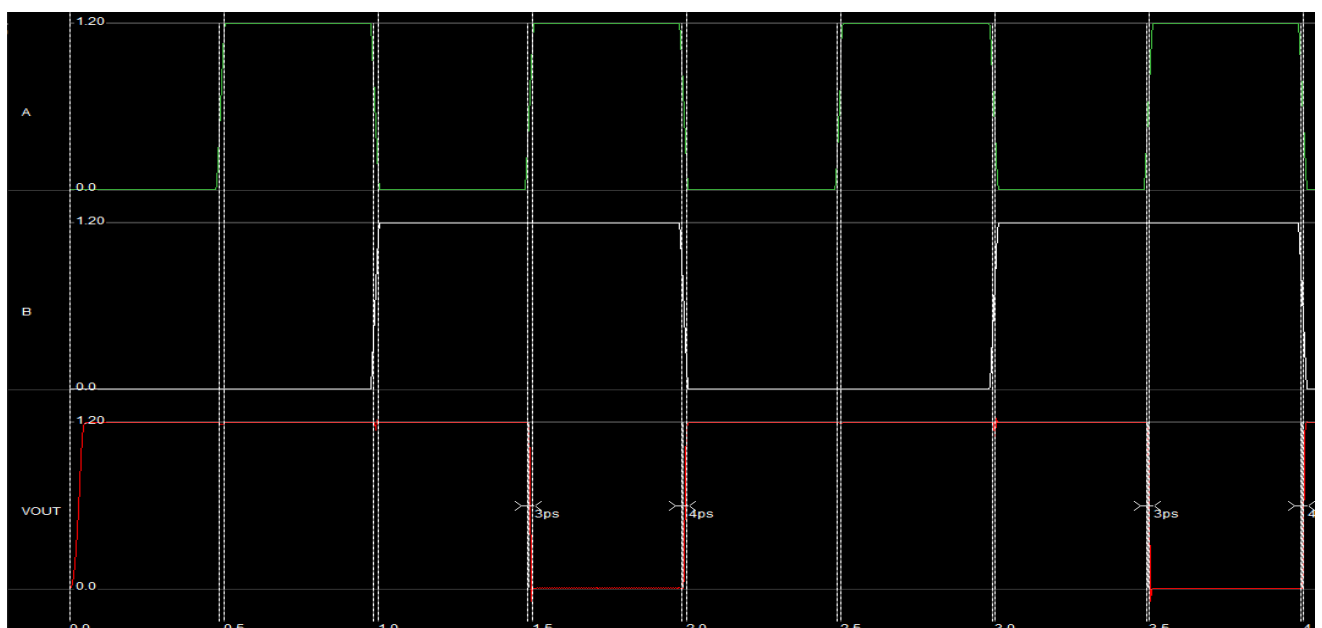


Output Waveform –



2:1 MUX using NAND Gates –

Design –

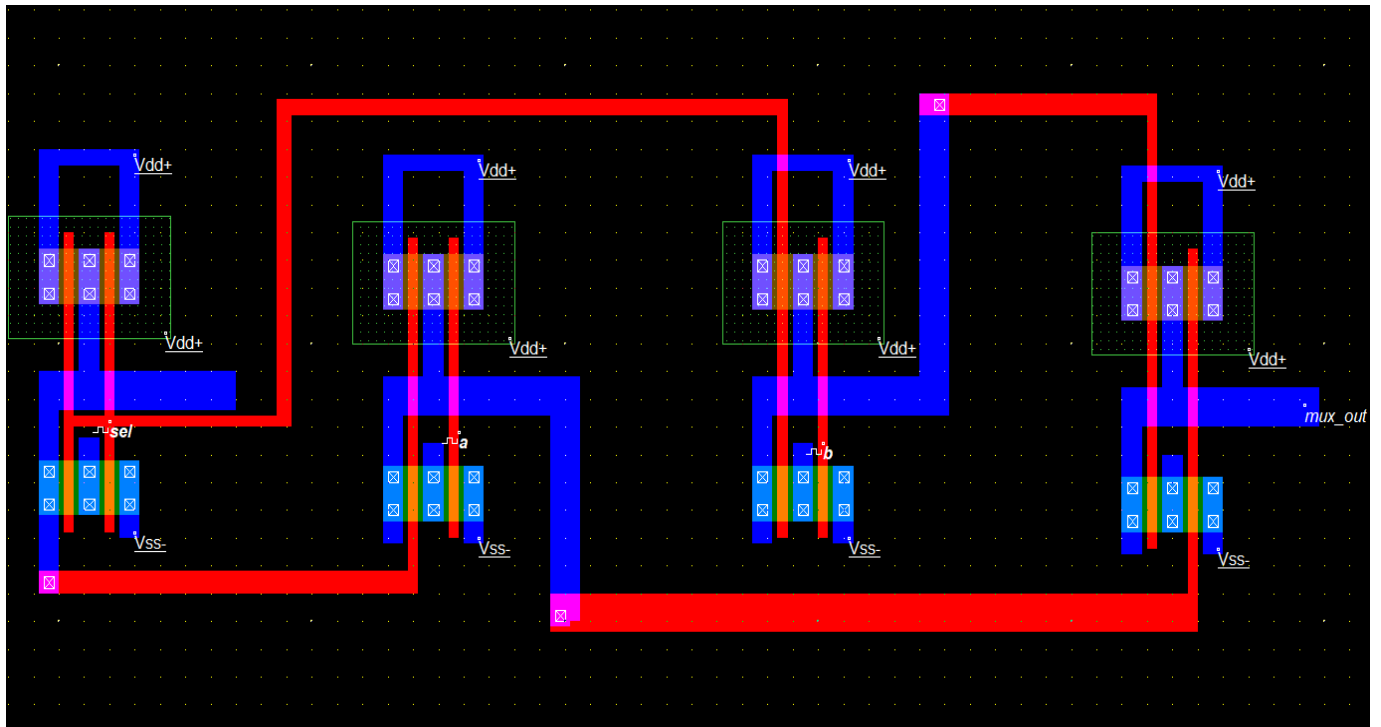

Output Waveform –

